

CSE 260M / ESE 260

Intro. To Digital Logic & Computer Design

Bill Siever
&
Michael Hall

This week


- Thursday: Studio – Need 1 Hw kit *and cable* for each group!
- Exam 1: Will be returned later this week
 - Midterm Grades on Canvas, etc. soon after
- Hw 4A probably returned too
- Hw 4B posted tonight:
 - Due Monday, March 18th @ 11:59pm (reading for ch 5 also due then!)

Chapter 4

Review: HDLs *Describe* Hardware


- Uses
 - Simulation: Confirm modules work together
 - “Synthesis” : Transformation to real hardware
 - Like compilers used for programming languages
- Use *modules* for hierarchical design — important part of managing complexity
- Description Styles
 - Structure (connect 2 input AND to ...)
 - Behavior (if x then y)

(System) Verilog Module: Review

 


```
module example(input logic a, b, c,  
                output logic y);  
    // module body goes here  
endmodule
```

 Input & Output
are like the Pins
On chips or in
JLS



(System) Verilog

 - Conditionals via Ternary operator (? :)




```
module mux2 (input logic [3:0] d0,  
              input logic         s,  
              output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```

Behavioral

8-bit mux2: Hierarchical
 
```
module mux2_8(input logic [7:0] d0, d1,  
               input logic      s,  
               output logic [7:0] y);  
  
    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);  
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);  
endmodule
```




Sequential Logic

always: Based on *Events*

- Concept of “event” is related to simulation and “event driven programming”
- JLS uses events: An OR gate “reacts” to events and schedules an update
See here

Discrete Time Event Simulator

 - Computes all activities / updates for “now”
 - They cause new activities that need to be handled in the future (at: now + prop delay). Those are put in a queue at for that time.
Ex: Update an or-gate’s output at now+4
- Move on to “now +1”, repeat



Discrete Time Event Simulator

- Updating values in current turn: Incrementally or all at once at end of turn
 - Ex: Assume x is 1 and y is 0
 - Incremental:
 $x = 0$
 $y = x$
 - All at once / end of turn
 $x \leq 0$
 $y \leq x$
 - x's final value is 0
y's final value is 0 too
 - x's final value is 0
y's final value is 1

SystemVerilog Standard

- Why all the simulation details?
- Quick intro to SystemVerilog Standard
 - Section 9 / 9.2

always Statement

- **Form:**

```
always @(sensitivity list)
    statement;
```

- **When event in sensitivity list occurs, statement is executed**
- **Ex:** always @(posedge clock)
 statement;
- **Verilog:** Don't use this in here

always Statement

- **Form:**

```
always @(sensitivity list)
    statement;
```

- **When event in sensitivity list occurs, statement is executed**
- **Verilog: *Don't use this in here***

always in 260

- Form 1: Comb logic

```
always_comb  
statement;
```

Use blocking assignment (=)

- Statement(s) are (complex) combinational logic. Like if/else or case.
Updates when any (relevant/used) input changes

- Form 2: Registered (synchronous, synthesizable, sequential) logic

```
always_ff @(sensitivity list)  
statement;
```

- Often @(posedge clock) used

Use non-blocking assignment (<=)

Assignments

- **Form 1: Continuous Assignment**

```
assign var = expression;
```

- Continuously assigned! Largely a wired connection

- **Forms 2 & 3 *in Procedures* (in some form of always*) :**

- **Blocking (=):** Will be “instant” in terms of simulation

- `always_comb`

- **Non-Blocking (<=):** Will occur at end of turn all at once

- `always_ff`

Rules for Assignments

- **Synchronous sequential logic**

use always_ff @(posedge clk) and nonblocking assignments (<=)
always_ff @(posedge clk)
q <= d; // nonblocking

- **Simple combinational logic**


use continuous assignments (assign)
assign y = a & b;

- **Complex Combinational Logic**

use always_comb and blocking assignments (=)


- **Assign signals in only one always or assign statement!**

Verilog: D Flip-Flop

 

```
module flop(input logic clk,  
           input logic [3:0] d,  
           output logic [3:0] q);  
    always_ff @(posedge clk)  
        q <= d; // pronounced "q gets d"  
endmodule
```


Resettable D-Flip-Flop 1

 

```
module flopr(input logic      clk,
              input logic      reset,
              input logic [3:0] d,
              output logic [3:0] q);

  always_ff @ (posedge clk)
    if (reset) q <= 4'b0;
    else        q <= d;
endmodule
```


Resettable D-Flip-Flop 2

 

```
module flopr(input logic clk,
              input logic reset,
              input logic [3:0] d,
              output logic [3:0] q);

  always_ff @ (posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else       q <= d;
endmodule
```

Resettable D-Flip-Flop 3

 

```
module flopr(input logic clk,
              input logic reset,
              input logic en,
              input logic [3:0] d,
              output logic [3:0] q);

    always_ff @ (posedge clk, posedge reset)
        if (reset)      q <= 4'b0;
        else if (en)    q <= d;
endmodule
```

always and Combinational Logic

Block of
assignments

```
always_comb
begin
    y = a & b
    ...
end
```

Could have
been done with
individual assigns

Notice = (“blocking assignment”),
not <= (“non-blocking assignment”)



always_comb has nice features

- **case** : Selection between several options
Great for state machines!
 - Must describe all possible combinations to be comb logic. Use default


```
case (state)
    soap:           hot = 1;
    highPressureWarm: hot = 1;
    ...
    default: hot = 0;
endcase
```

Verilog FSMs

  - Three parts
 - Next state logic
(arrows / next state table)
 - State register (active bubble)
 - Output logic (output equations)



Divide by 3 Counter

 

Verilog


```
module divideby3FSM(input logic clk,
                     input logic reset,
                     output logic q);

    typedef enum logic [1:0] {S0, S1, S2} statetype;
    statetype state, nextstate;

    // state register
    always_ff @(posedge clk, posedge reset)
        if (Treset) state <= $0;
        else state <= nextstate;

    // next state logic
    always_comb
        case_(state)
            S0:    nextstate = S1;
            S1:    nextstate = S2;
            S2:    nextstate = S0;
            default: nextstate = S0;
        endcase

     // output logic
    assign q = (state == S0);
endmodule
```



Parameterized Modules: Declaration

- Way to specify additional details for an *instance* of a generic part
 - Commonly the “width” of the part

```
module mux2
#(parameter width = 8) // name and default value
  (input logic [width-1:0] d0, d1,
   input logic           s,
   output logic [width-1:0] y);
  assign y = s ? d1 : d0;
endmodule
```

Parameterized Modules: Use

- Default or specify parameter for instance:

```
mux2 myMux(d0, d1, s, out);
```

```
mux2 #(12) lowmux(d0, d1, s, out);
```

Ports: Positional vs. Named

- Default or specify parameter for instance:

```
logic a, b, see, y  
mux2 myMux(a, b, sel, y);
```

vs.

```
mux2 myMux(.d0(a), .d1(b),  
           .s(sel), .out(y));
```

```
module mux2  
#(parameter width = 8)  
  (input logic [width-1:0] d0,  
   input logic s,  
   output logic [width-1:0] y)  
  assign y = s ? d1 : d0;  
endmodule
```

Test Bench: Overview & Concept (Simple w/ Asserts)

Hw4A: simple_comb_tb

FPGA: Field Programmable Gate Array

FPGA


- Field Programmable
- Gate Array
 - Lattice iCE40 UP5k: Architecture Overview
 - RAMs, (Dual and Single Port)
 - Look Up Tables (LUTs): 4 inputs
 - D Flip Flops
 - Lots: ~5,000

Playground: Combinational logic, hardware, synthesis, and parameters


Questions

Adders

Half
Adder

 

Full
Adder

 

A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\begin{aligned}S &= A \oplus B \\C_{\text{out}} &= AB\end{aligned}$$

C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned}S &= A \oplus B \oplus C_{\text{in}} \\C_{\text{out}} &= AB + AC_{\text{in}} + BC_{\text{in}}\end{aligned}$$

Ripple Carry Adder: Propagation Delay

